



Welcome to The Hardware Lab!

Fall 2018
Behavioral Modeling

Prof. Chun-Yi Lee

Department of Computer Science
National Tsing Hua University

Agenda

- **Announcement**
- **Behavioral modeling**
 - **Behavioral constructs**
 - **Procedural statements**

Today's class will help you:

1. Understand the the difference between structural modeling and behavioral modeling
2. Understand how to use always block and its applications
3. Understand the difference of blocking and non-blocking assignments
4. Understand how to correctly use procedural statements in behavioral modeling

Announcement

- Lab
 - Lab 2 Verilog submission due on **10/4/2016 (Thu)**
 - Lab 2 FPGA demonstration due on **10/4/2016 (Thu)**
- Assistance:
 - During the lab hours
 - TA hour: after the lectures (19:00~21:00) on Tuesdays
 - Please make a reservation in advance
<https://goo.gl/forms/Mfl2Y1erpw6b71Wf2>

Agenda


- Announcement
- Behavioral modeling
 - Behavioral constructs
 - Procedural statements

Today's class will help you:

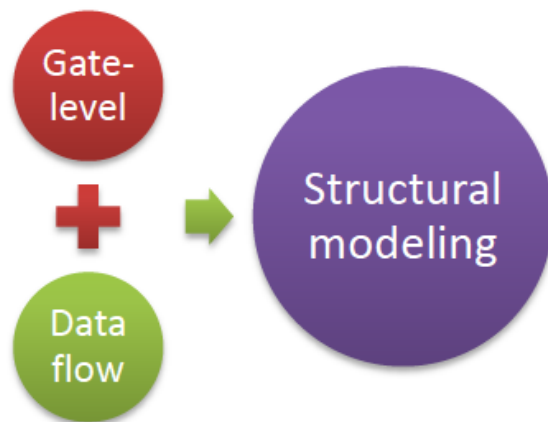
1. Understand the the difference between structural modeling and behavioral modeling
2. Understand how to use always block and its applications
3. Understand the difference of blocking and non-blocking assignments
4. Understand how to correctly use procedural statements in behavioral modeling

Behavioral Modeling

- High level description
- Modeling a circuit by its behaviors
- Similar to C++ programming
- Behavioral modeling includes both **combinational** and **sequential** parts



Combinational only

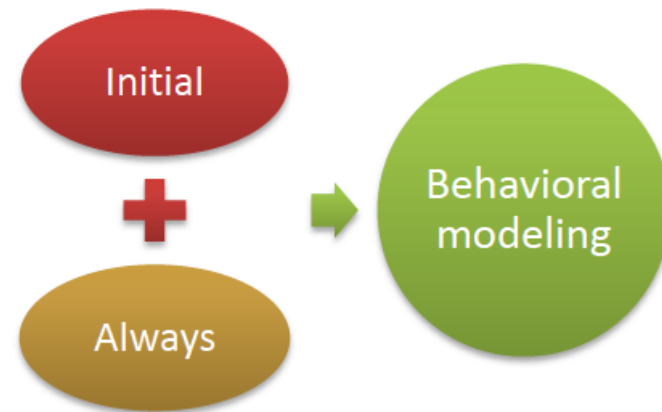

Combinational and Sequential

Structural vs. Behavioral Modeling

Structural modeling

```
module My_Module(...);
```

```
...
```

```
assign O1 = A+B;
```

```
and N1(O2, C, D);
```

```
MUX M1(O3, Sel, F, G);
```

```
// 1. continuous assignment
```

```
// 2. Instantiation of a primitive
```

```
// 3. Instantiation of a module
```

Behavioral modeling

```
always @ (...)
```

```
begin ... end
```

```
// 1. Always block
```

```
initial
```

```
begin ... end
```

```
// 2. initial block
```

```
// initial only used in testbench
```

```
endmodule
```

Behavioral Constructs

- Two constructs: **initial** and **always**
- Similar point:
 - lvalue has to be of **reg** data type
 - Has **begin** and **end**
- **initial:**
 - Used in testbench only
 - Only run once when the testbench begins
- **Always**
 - Used both in design and testbench
 - Repeated execution


Initial Block

- In your **testbench only**
- **NOT** synthesizable
- Run once in the beginning (**time 0**)

```
...  
initial                                // An "initial" behavior  
    begin  
        A = 1'b0;                        // Procedural assignments  
        B = 1'b1;                        // execute sequentially  
        #20  
        C = 2'b11;  
    end  
...
```


Register Transfer Level

 - Describes the behavior of combinational circuits between registers



Always Block

- Two types of always block


Combinational circuit

```
reg A, B, C;  
  
always @ (A or B)  
begin  
    //Blocking Assignment  
    B = A;  
    C = B;  
end
```



Sequential circuit
 
```
reg A, B, C;  
  
always @ (posedge clk)  
begin  
    //Non-blocking assignment  
    B <= A;  
    C <= B;  
end
```



Blocking and Non-blocking

Execute in Order


```
always @ (A or B or C)  
begin
```

```
    //Blocking Assignment
```

```
    C = A & B;
```

```
    D = !C;
```

```
end
```

 

Execute in Parallel


```
always @ (posedge clk)  
begin
```

```
    //Non-blocking assignment
```

```
    C <= A & B;
```

```
    D <= !C;
```

```
end
```

 

- **NEVER** use blocking and non-blocking assignment in the **SAME** always block

Caution for Always Block

- Combinational circuit: use blocking assignment (=) only

```
always @ (A or B or C)
begin
    //Blocking Assignment
    C = A & B;
    D = !C;
end
```

- Sequential circuit: use non-blocking assignment (<=) only

```
always @ (posedge clk)
begin


    //Non-blocking assignment
    C <= A & B;
    D <= !C;
end
```

Bad and Good Examples




// blocking assignment

```
always @(posedge clk) begin
  M = A & B;
  Y = M | C;
end
```

 

// non-blocking assignment

```
always @(posedge clk) begin
  M <= A & B;
  Y <= M | C;
end
```

 

Sensitivity List

- Wakes up an always block and do the execution
- **For combinational circuit only**
- Separated by **or**
- Variables include:
 - Right hand side of "="
 - Condition variables in **if**
 - Condition variables in **case**

```
always @ (A or B or C or Sel or Sel_Bus)
begin
    C = A & B;

    if (Sel) begin
        D = !C;
    end

    case (Sel_Bus)
        .....
    endcase
end
```

- No need of sensitivity list for **always @(*)**

Caution of Assignments



```
// Error version
module FullAdder(s, co, a, b, ci);
```

```
input a, b, ci;
```

```
output s, co; Error continuous  
assignment!
```

```
s = a ^ b ^ ci;
```

```
always @(a or b or ci) begin
```

```
  assign co = (a&b)|(b&ci)|(a&ci);
```

```
end
```

```
endmodule
```

Error procedural
assignment!



```
// Correct version
```

```
module FullAdder(s, co, a, b, ci);
```

```
input a, b, ci;
```

```
output s, co;
```

```
reg co; ← value of procedural  
assignment must be reg
```

```
assign s = a ^ b ^ ci;
```

```
always @(*) begin
```

```
  co = (a&b)|(b&ci)|(a&ci);
```

```
end
```

```
endmodule
```


Agenda

- Announcement
- **Behavioral modeling**
 - Behavioral constructs
 - **Procedural statements**

Today's class will help you:

1. Understand the the difference between structural modeling and behavioral modeling
2. Understand how to use always block and its applications
3. Understand the difference of blocking and non-blocking assignments
4. Understand how to correctly use procedural statements in behavioral modeling

Procedural Statements

- Control operators similar to C++
- Not all of the operators can be used in your design
- Any operator used in the design must be **synthesizable**
 - However, you can use non-synthesizable operators in testbenches

Operator	Design	Testbench	Synthesized to
If-else	Yes	Yes	Mux
case	Yes	Yes	Mux or Decoder
for	No	Yes	N/A
while	No	Yes	N/A
repeat	No	Yes	N/A

If-Else Statement


```
if (condition1)
  begin
    <expression> ;
  end
else if (condition2)
  begin
    <expression> ;
  end
else
  begin
    <expression> ;
  end
end
```

```
module MUX3(out, a, b, sel);

output    out;
input     a,b,sel;
reg       out;

always @(*) begin
  if(sel == 1'b1)
    out = a;
  else
    out = b;
end


endmodule
```

 

Synthesized to a **MUX**

Case Statement
 
```
case (condition)
  alternative1: <expression> ;
  alternative2: <expression> ;
  ...
  default: <expression> ;
endcase
```



Synthesized to a **MUX**

```
module mux4to1 (out, in, sel);

  output      out;
  input [3:0] in;
  input [1:0] sel;
  reg         out;

  always @(*) begin
    case (sel)
      2'd0 :      out = in[0];
      2'd1 :      out = in[1];
      2'd2 :      out = in[2];
      default :   out = in[3];
    endcase
  End

endmodule
```

Case Statement (Cont'd)



Din[1:0]	Dout[3:0]
00	0001
01	0010
10	0100
11	1000

Synthesized to a **DECODER**

```
module mux4to1 (out, in, sel);

output [3:0]  Dout;
input  [1:0]  Din;
reg    [3:0]  Dout;


always @(*) begin
    case (Din)
        2'd0 :      Dout = 4'b0001;
        2'd1 :      Dout = 4'b0010;
        2'd2 :      Dout = 4'b0100;
        default :    Dout = 4'b1000;
    endcase
End

endmodule
```

Unintended Latch

- **Clearly specify** every situations in **if-else** or **case** statements
- Incomplete statements lead to **unintended latch**
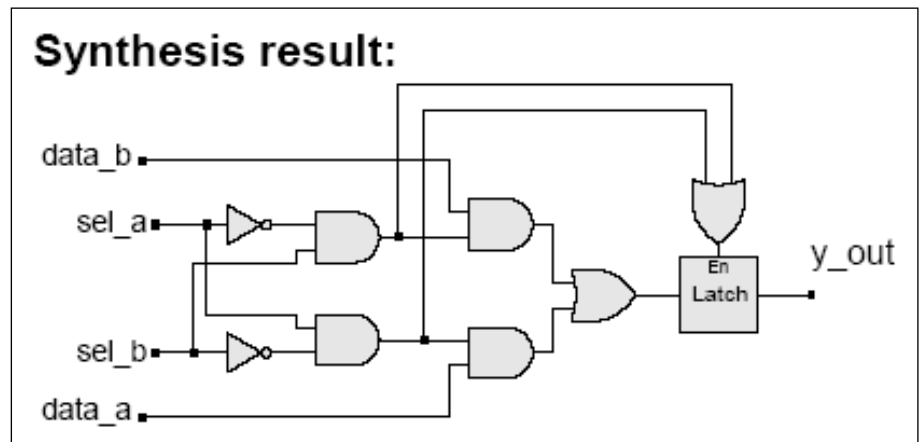
```
always @ (sel_a or sel_b or  
          data_a or data_b)  
begin  
  
    case ({sel_a, sel_b})  
        2'b10: y_out = data_a;  
        2'b01: y_out = data_b;  
    endcase  
  
end
```



Loop Statements

- Not synthesizable
- Used in testbench only

For loop

```
reg [15:0] x;  
integer i;  
  
initial  
begin  
    x = 16'd0;  
    for ( i = 0; i <= 10; i = i + 1 )  
    begin  
        x[i+1] = 16'd0;  
        x[i+2] = 16'd1;  
    end  
end
```

Repeat loop

```
reg [15:0] x;  
  
initial  
begin  
    x = 16'd0;  
    repeat ( 16 )  
    begin  
        #2  
        x = x + 1'b1;  
    end  
end
```

While loop

```
reg [15:0] x;  
  
initial  
begin  
    x = 16'd0;  
    while ( x <= 20 )  
    begin  
        #2  
        x = x + 1'b1;  
    end  
end
```


Constants

- Declare with keyword parameter
- Similar to **const** in C++
 - On the other hand, **`define** is similar to **#define** in C++
- Value does not change during simulation
- Can be used in vector declaration
 - Easier in project development and maintenance

```
parameter size = 16;  
    reg [size-1:0] a; // vector declaration  
parameter b = 2'b01;  
parameter av_delay = (min_delay + max_delay) / 2;
```


Delay Control Operator

- **#** followed by units of time
- Specify the delay in terms of units specified by ``timescale`
- NOT synthesizable, only used in testbench
- In real circuits, delay is realized by buffers (two inverters)

```
...  
always  
begin  
    #0    clock = 0;  
    #50   clock = 1;  
    #50;  
end  
...
```

```
...  
always  
begin  
    #clock_period/2;  
    clock = ~clock;  
end  
...
```

parameter
clock_period



Thank you for your attention!



*Reno Air Balloon Festival taken at Reno, Nevada, USA.
This picture is taken by Chun-Yi Lee himself, who is also a fan of photography